

ECE6703J

Computer-Aided Design of Integrated Circuits

Timing Analysis

Outline

- Timing Analysis: Basics, Assumptions, and Models
- Static Timing Analysis: Basic Idea


ASIC Timing: Role of CAD Tools

- ASIC timing has **deep interactions** with logic and layout synthesis.

High-level description
+ **Timing Specifications**




Logic
Synthesis

 

Connected cells with
delay constraints on
signal paths


Layout
Synthesis

 

Placed cells
with real locations,
real connecting wires

ASIC Timing: Role of CAD Tools

 - Requirement on timing analysis
 - Logic-side tools must **estimate delays** through unplaced/unrouted logic.
 - Layout-side tools must **estimate delays** through placed/routed logic.



Our Topics for ASIC Timing


- Logic-side: **Static Timing Analysis**
 - How do we estimate the worst-case timing through a logic network?
 - Turns out to be **longest paths** through a graph that properly models the gates and wires.
- Layout-side: **Interconnect Delay Analysis**
 - We place the gates, route the wires. Then, how do we estimate **wire delays**?
 - The problem is built up on electrical circuit model. We will show key methods.

Timing Analysis at the Logic Level

- Goal: Verify timing behavior of our logic design
- Input:
 - A gate-level netlist.
 - **Timing models** of the gates and/or wires.
- Output:
 - **Signal arrival time** at various points in the network.
 - **Longest delays** through gate network.
 - Does the netlist **satisfy** the timing requirement? If not, where are the key problems?
- This is surprisingly complicated in the real world...


Assumption: Design Is Synchronous

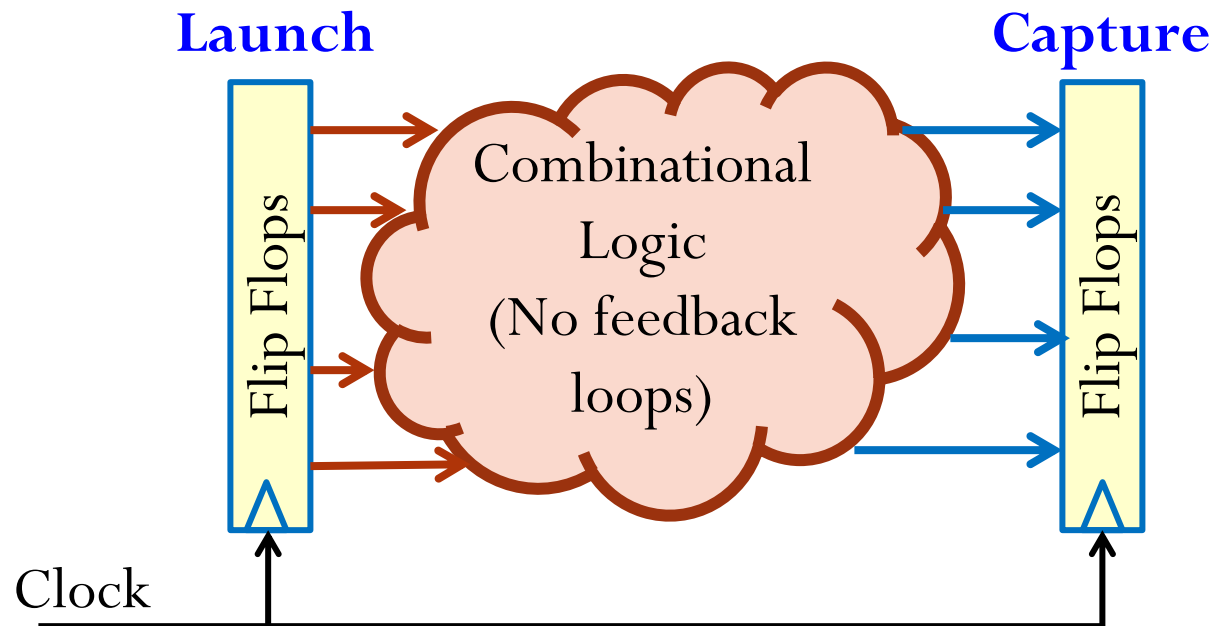- All storage is in explicit sequential elements, e.g., flip-flop elements.
- Consequence: we can just focus on delays through combinational gates.




Timing Analysis: Basic Model

 - Assume we know clock cycle
 - E.g., 1GHz clock, cycle = 1ns.



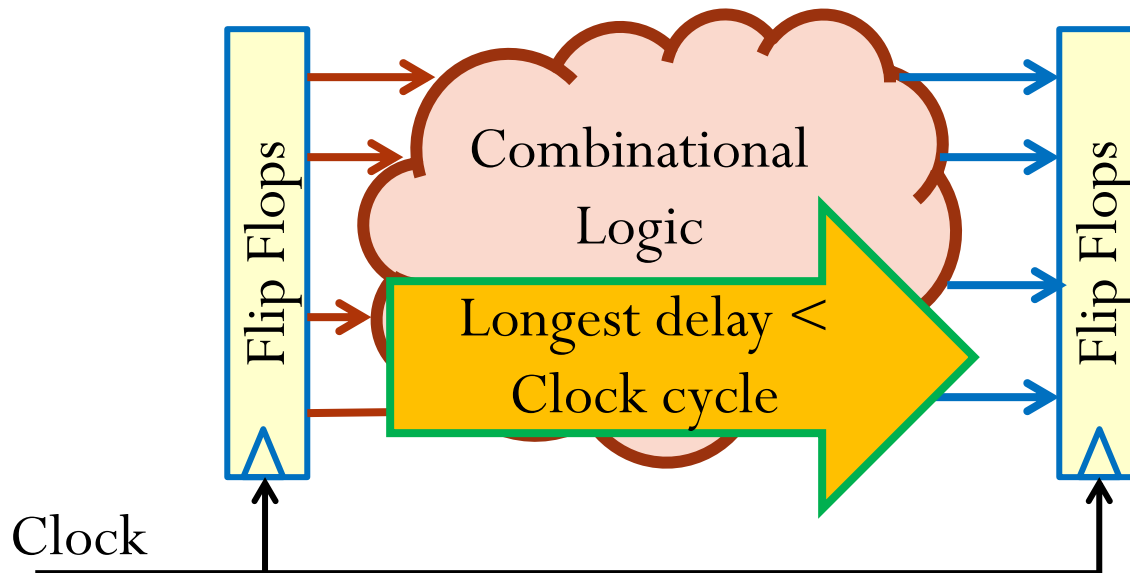- For logic to work **correctly**, **longest delay** through network must **be shorter than the clock cycle**.




Question: Can't We Just Simulate Logic?



- What logic simulation does?
 - Determines how a system will behave by simulating the netlist.
 - Gives the most **accurate** answer with good simulation models.
 - ... but it is (practically) impossible to give a complete answer — especially timing.
- Requires examination of an **exponential** number of cases.
 - All possible input vectors ...
 - With all possible relative timings ...
- We need a **different, faster** solution...

Timing Analysis: Gate Delay Models

 - First: we need a model of delay through each logic gate.



- Delay of a single gate:

 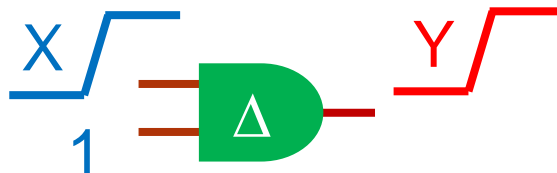


In Reality: Gate Delay is Very Complex



- Gate **type** affects delay



- Gate **loading** affects delay

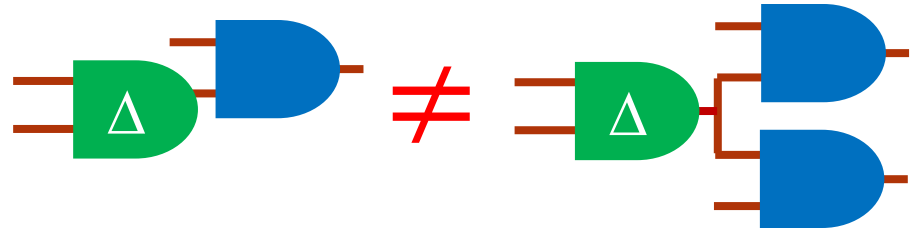


  - Waveform shape** affects delay
- Transition direction** affects delay




In Reality: Gate Delay is Very Complex

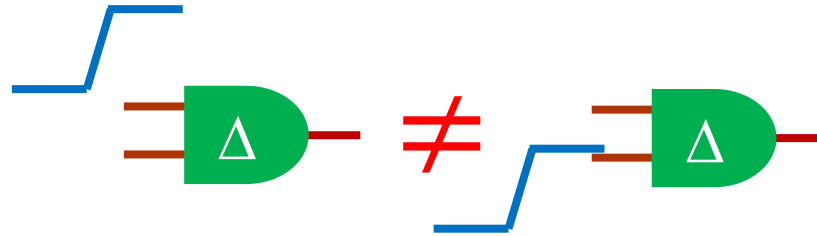- Gate **input pin** affects delay
 - Why? At transistor level, inputs are not symmetric.




 - At nanoscale, delays are even **statistical**
 - Why? Depends on process, voltage, and thermal (PVT) variations.




Our Model: Pin-to-Pin Delay

 - In our lecture, we keep it simple: **Fixed, pin-to-pin delay model**
 - No waveform, transition direction, distributions. Loading effects “pushed” into gate delay itself.
 - Per-pin delays are essential, but we will use **just 1 value per gate**, for simplicity.
 - Turns out this is enough to see all the interesting algorithm ideas.



Do We Consider Logical Function?

 - Does logic function matter?
- Try an example, where we “erase” gates.
 - In this example: **PI** = Primary Input, **PO** = Primary Output




What is the longest delay?

20

Now, Suppose We Know Logic Gates

Can we indeed have the longest path?

No!

 

- We cannot **sensitize** this path: cannot make a logic change at this input propagate down this path to change this output.

Topological vs Logical Timing Analysis


- When we ignore logic, this is called **Topological Analysis**.
 - We only work with graph and delays, **don't** consider logic.
 - We can get wrong answers: what we found was called a **False Path**.
 - This gives an upper bound
- Going forward: we **ignore logic** (Too tough to deal with)
 - Assume that all paths are **sensitizable**.
- This timing analysis has a name: **Static Timing Analysis (STA)**.

Outline

- Timing Analysis: Basics, Assumptions, and Models
- Static Timing Analysis: Basic Idea


STA Representation: Delay Graph

 - From gate-level network, we build a **delay graph**.
 - Vertices: **Wires** in gate network, one per gate output, also one for each PI.
 - Edges: Input pin to output pin of **gate** in network (one edge per input pin). Put gate delays on edges.





Delay Graph

 - Common convention: Add **Source/Sink** nodes
 - Add one “**source**” (**src**) node that has a **0-weight edge to each PI**.
 - Add one “**sink**” (**snk**) node that has a **0-weight edge from each PO**.
- Why do this?
 - Now, the network has exactly **1** “entry” node, and **1** “exit” node.
 - All the longest (or shortest) path questions have same start/end nodes.




Delay Graph

  - What about **interconnect** delay?
 - Can still use delay graph: model each wire as a “special” gate that just has a **delay**.



Operations on Delay Graph

 - So how do we use delay graph to do **timing analysis**?
 - What we **don't** do: Try to enumerate all the source-to-sink paths.
 - Why not? **Exponential** explosion in number of paths, even for small graph.




How many paths
from node 0 to n?

2^n

- There's a smarter answer: **Node-oriented** timing analysis
 - Find, for **each node** in delay graph, **worst** delay to the node **along any path**.


Define Values on Nodes in Delay Graph

 - **ArrivalTime** at a node (AT)
 - $AT(n) = \text{Latest time the signal can become stable at node } n.$
 - Think: **Longest path from source**
- **Required ArrivalTime** at node (RAT)
 - $RAT(n) = \text{Latest time in cycle where } n \text{ could change and signal would still propagate to sink before end of cycle.}$
 - Think: **Longest path to sink**



Difference between ATs and RATs

- Look at clock cycle

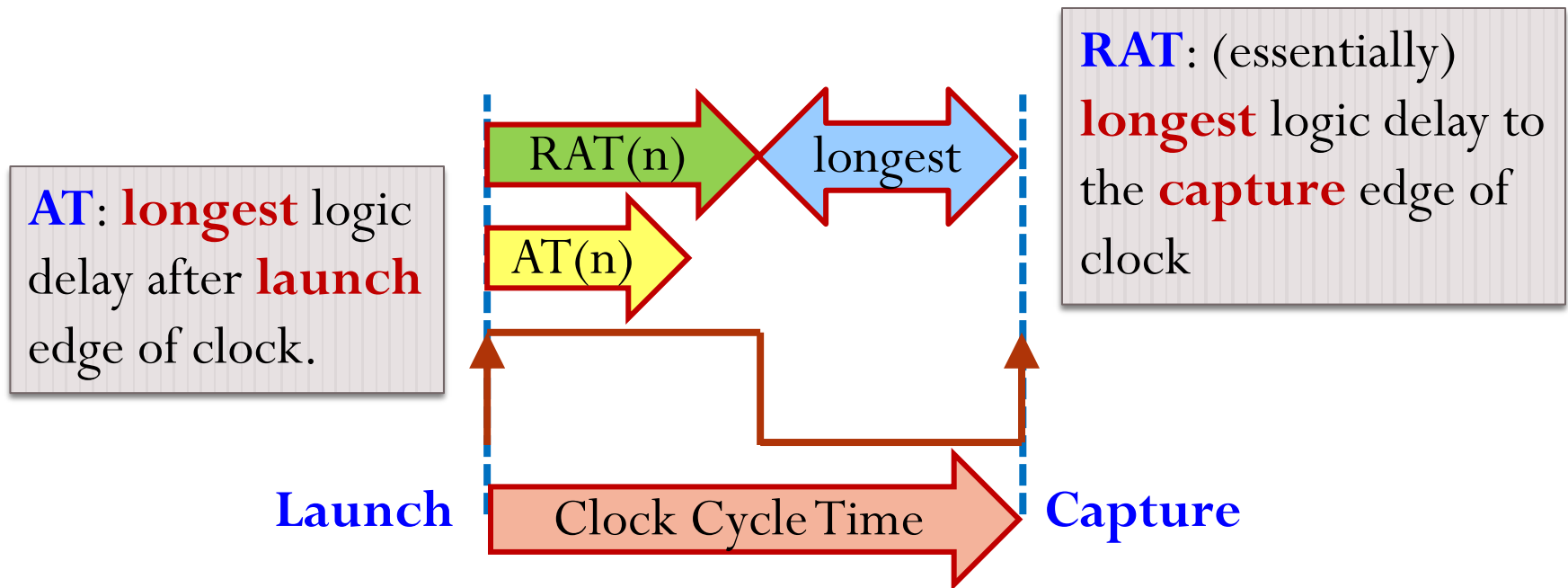


RAT < AT is BAD!

RAT < AT!




RAT - AT is **negative**!

Slack

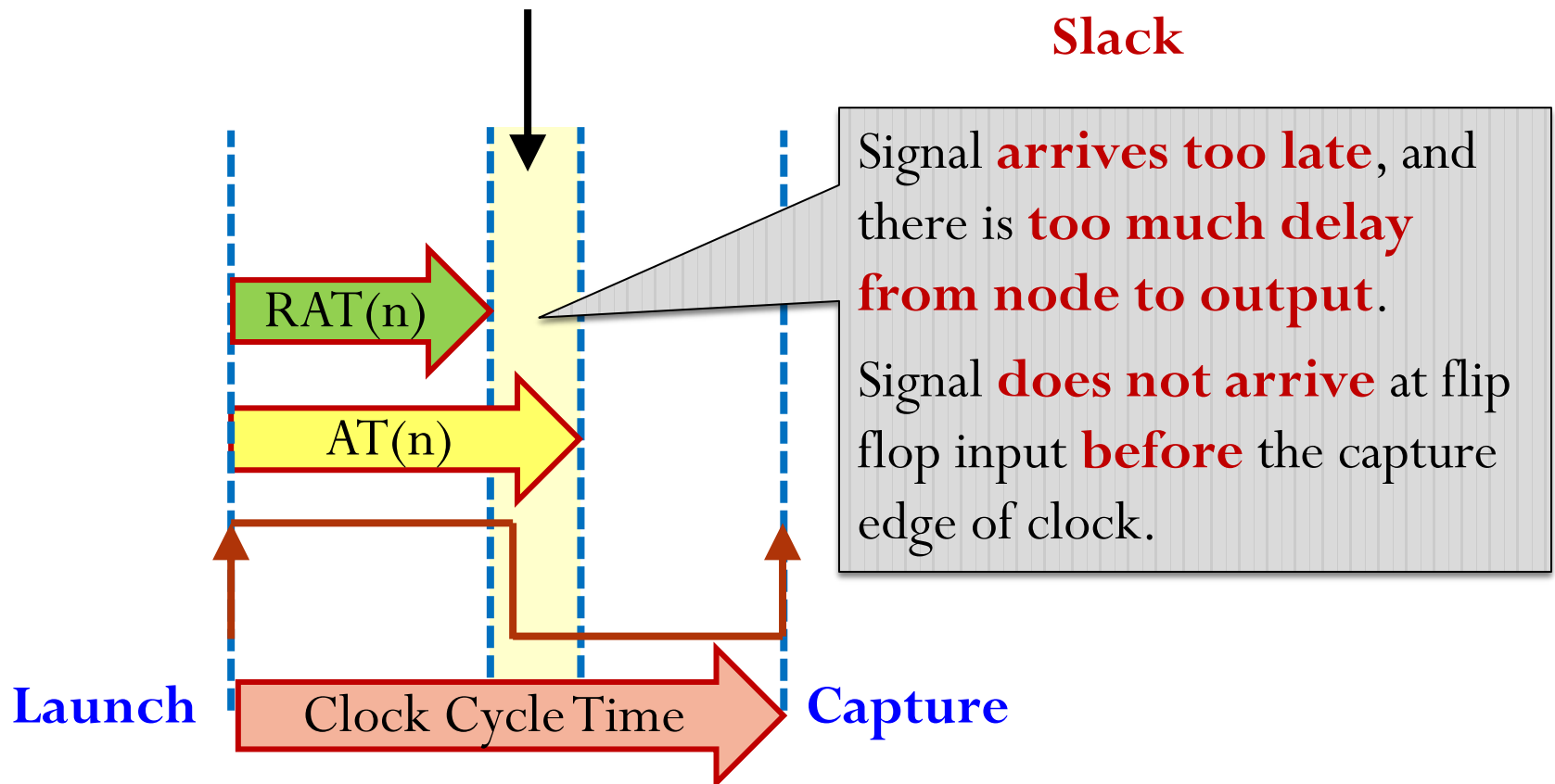

Slack

 - **Slack** at node n : $\text{Slack}(n) = \text{RAT}(n) - \text{AT}(n)$
 - Amount of timing “margin” for the signal: positive is good, negative is bad.
 - Determined by **longest** path **through** node.
 - Measures “**sensitivity**” of network to this node’s delay.




$$\text{Slack}(n) = \text{RAT}(n) - \text{AT}(n)$$

Slack is Hugely Important in Timing Analysis

- Positive slack
 - **Good**: Amount by which a signal can be **delayed** at node and **not increase** the **longest path** through the network.
 - Can change something at this node, and not hurt network's overall timing.
 - Example: make this node slower, maybe save some power, not hurt timing.
- Negative slack
 - **Bad**: have problem at this node; more negative the slack, bigger the problem.
 - Looking for a node to “fix” to help timing? These nodes are where to look first. These affect the critical paths the most.


How To Compute ATs? Recursively

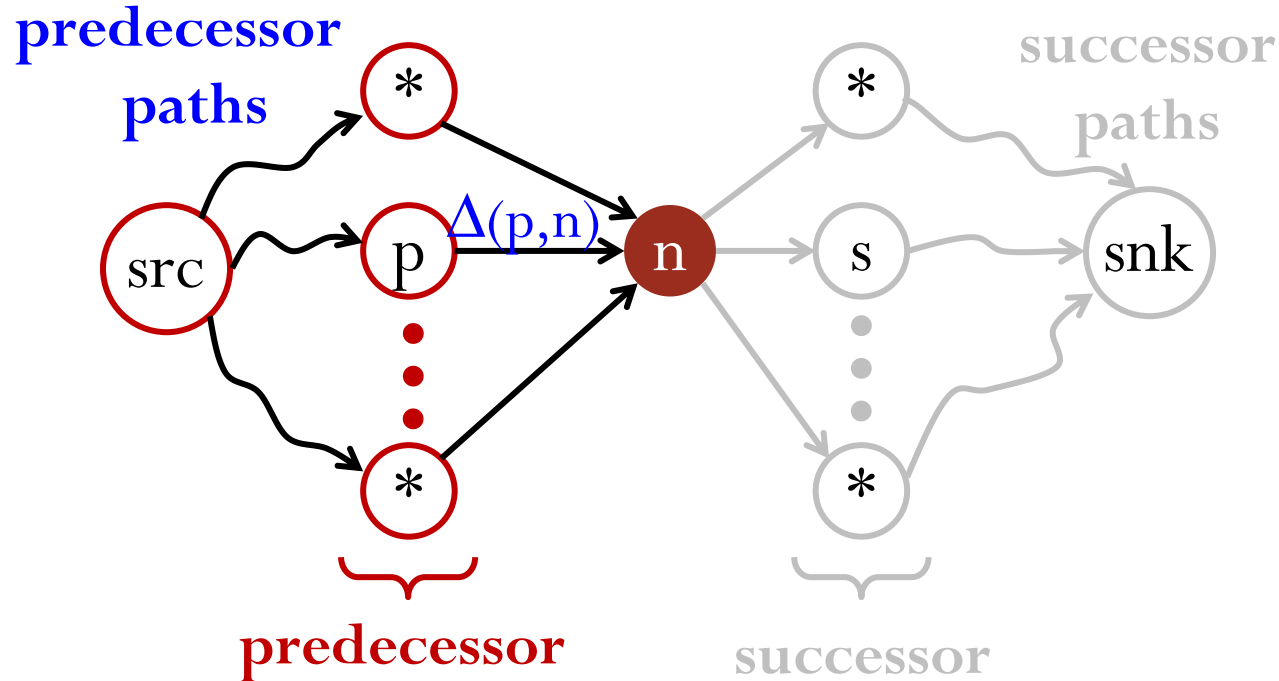

$$AT(n) = \text{maximum delay to } n = \begin{cases} 0, & \text{if } n \text{ is source} \\ \max_{p \in \text{prec}(n)} \{AT(p) + \Delta(p,n)\}, & \text{else} \end{cases}$$


How To Compute ATs?

 - Big idea
 - If we know the longest path to each predecessor of **n**, it's a simple “**Maximum**” operation to compute the longest path to **n** itself.




$$\begin{aligned} AT(n) &= \max_{p \in \{x,y,z\}} \{AT(p) + \Delta(p,n)\} \\ &= \max \{5+7, 10+1, 5+5\} \\ &= 12 \end{aligned}$$

How To Compute RATs?

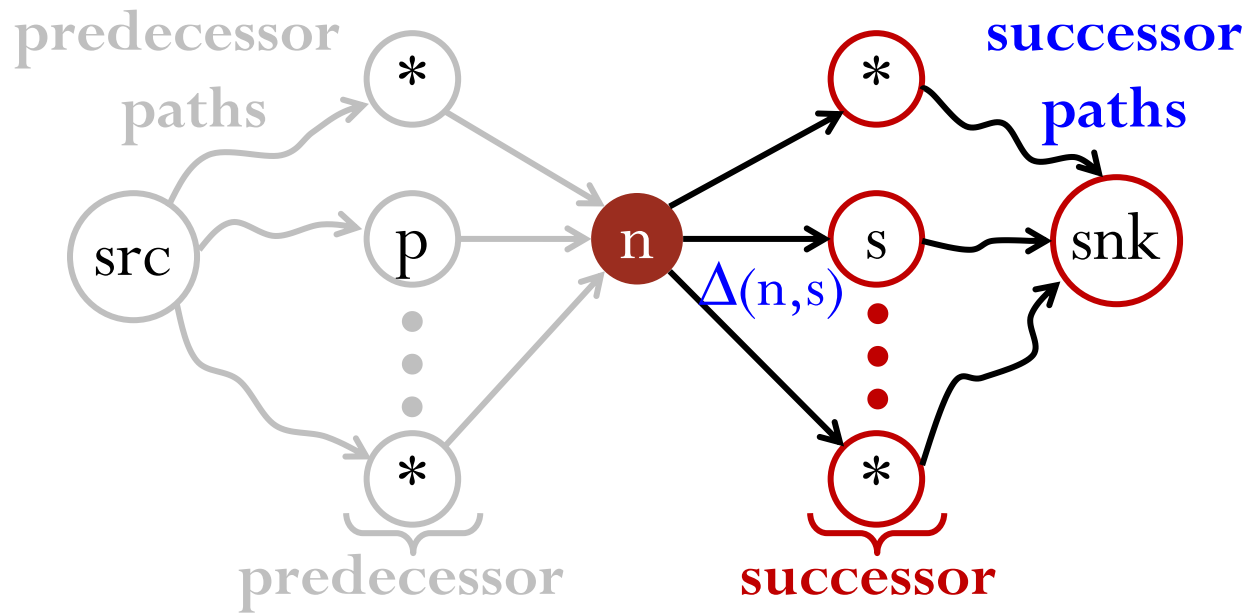

- $RAT(n)$: **Latest time** in cycle where n could change and signal would still propagate to sink before end of cycle.
- First, what is $RAT(sn_k)$? $RAT(sn_k) = \text{Cycle Time}$
- How about internal node n ? $RAT(n) = \min_{s \in \text{succ}(n)} \{RAT(s) - \Delta(n,s)\}$


How To Compute RATs? Recursively

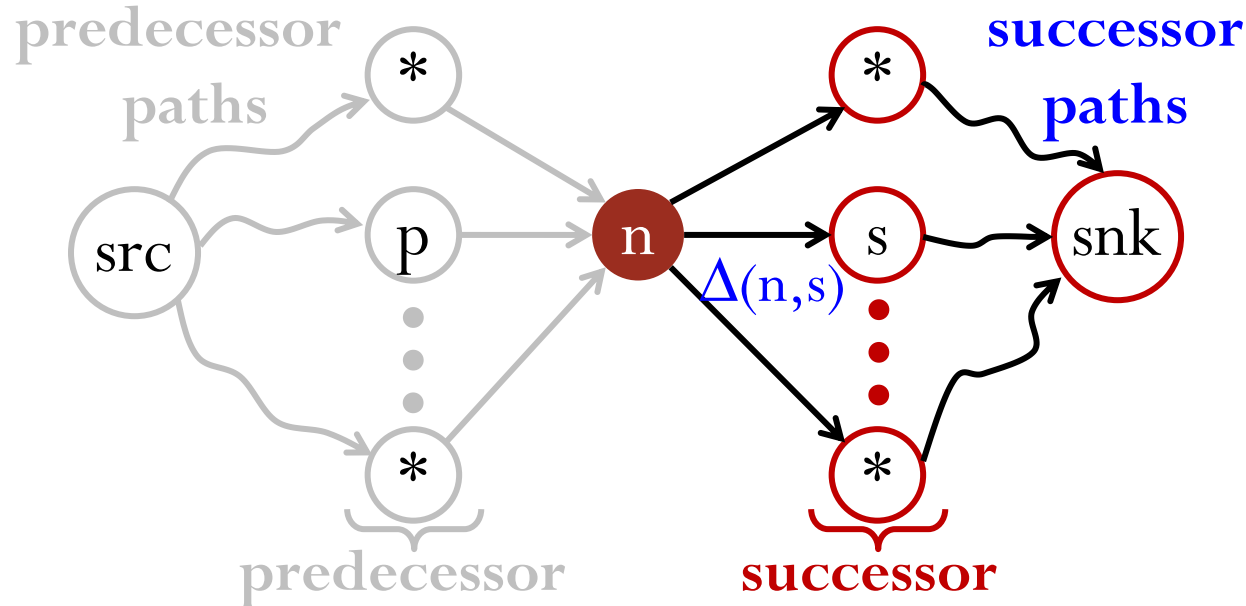

$$\text{RAT}(n) = \begin{cases} \text{Cycle Time,} & \text{if } n \text{ is sink} \\ \min_{s \in \text{succ}(n)} \{ \text{RAT}(s) - \Delta(n,s) \}, & \text{else} \end{cases}$$

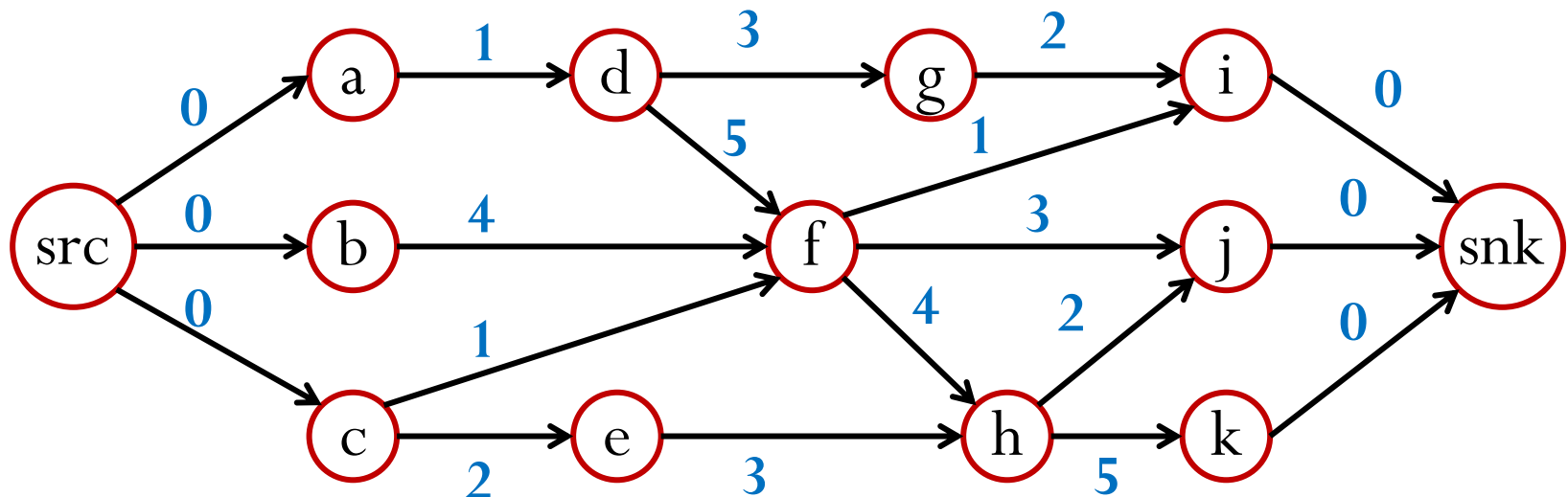Example


- Suppose clock cycle is 12.
- **AT**=longest path from source **TO** node.
- **RAT**=(cycle time 12) – (longest path **FROM** node to sink).
- **Slack** = **RAT** – **AT**



Compute ATs

$$AT(n) = \begin{cases} 0, & \text{if } n \text{ is source} \\ \max_{p \in \text{prec}(n)} \{AT(p) + \Delta(p, n)\}, & \text{else} \end{cases}$$

Compute ATs from src to snk

 


Compute RATs

- Clock cycle is 12.


$$\text{RAT}(n) = \begin{cases} \text{Cycle Time,} & \text{if } n \text{ is sink} \\ \min_{s \in \text{succ}(n)} \{ \text{RAT}(s) - \Delta(n,s) \}, & \text{else} \end{cases}$$

Compute RATs from snk to src

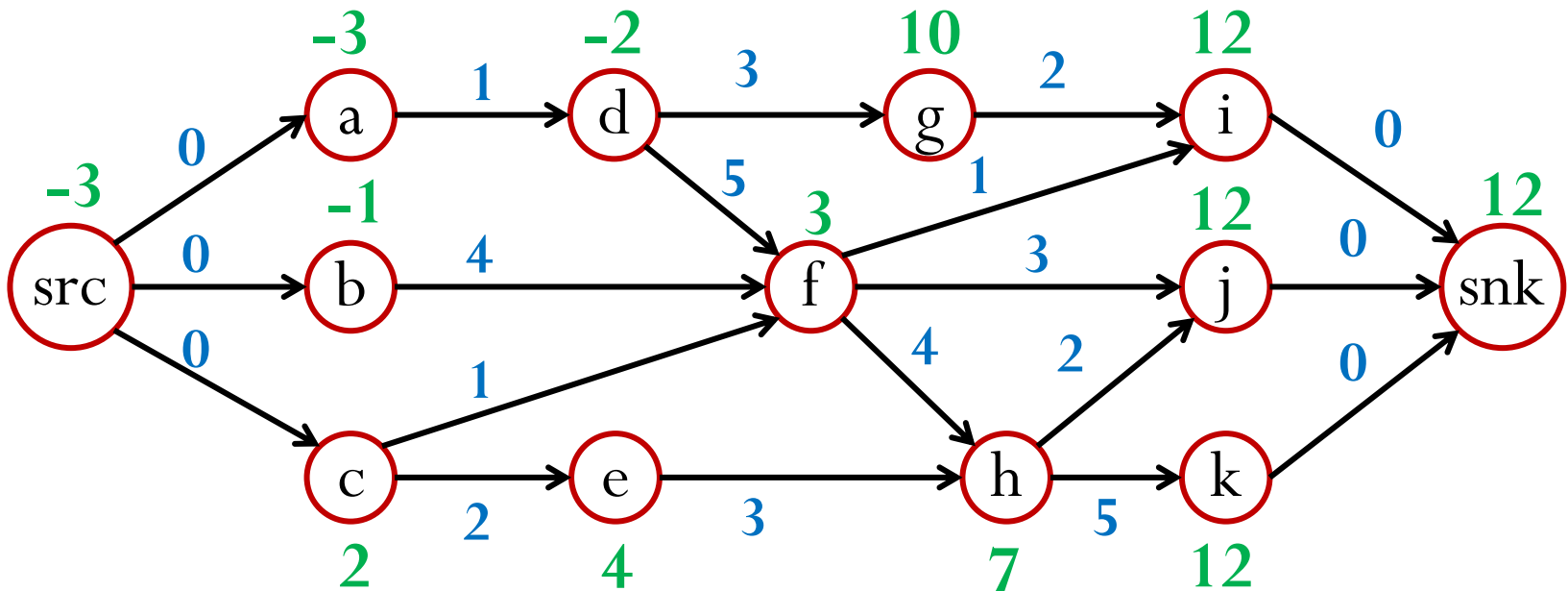


Compute Slack

- Slack = $RAT - AT$

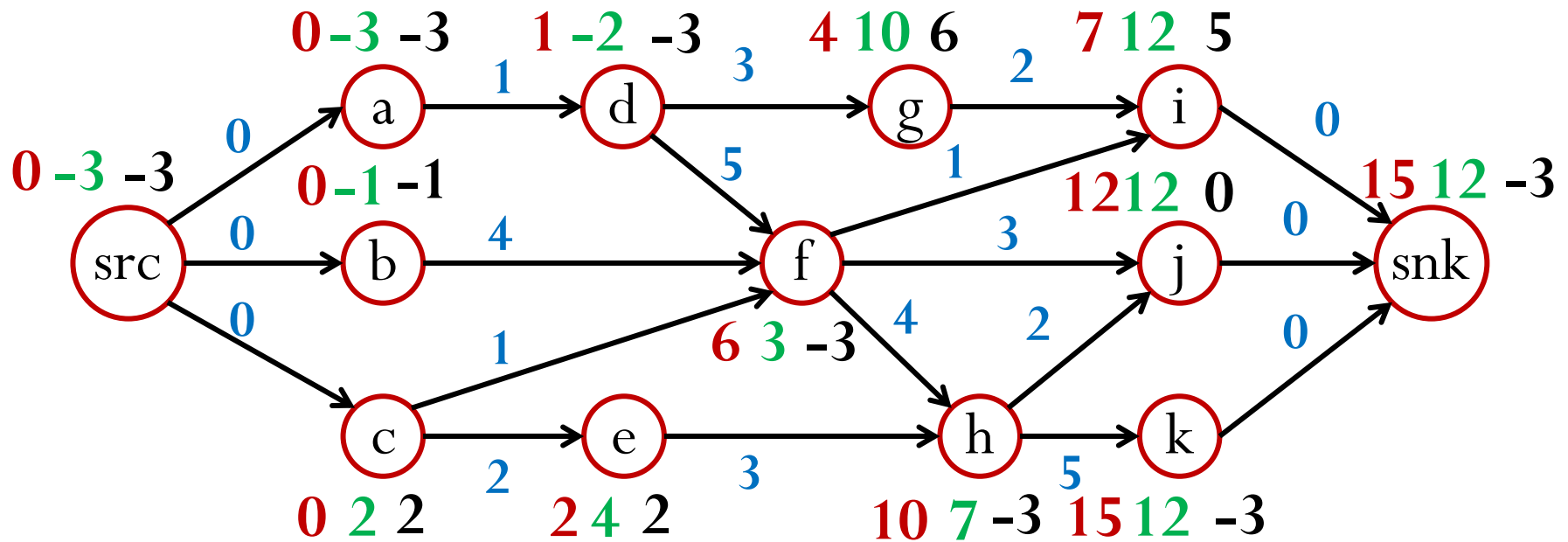

Analyzing the Example

 - Worst (most negative) slack is -3.
- Big results:
 - Your timing violation at sink = the worst slack value.
 - The worst slack appears along the **entire worst path**.



Analyzing the Example

- Look at those slacks
 - A negative slack at an output (PO) means a **failed** timing requirement.
 - A negative slack on internal node **n** means there is a path which has problem from some PI to some PO going through **n**.
- So, slacks are **hugely useful**!
 - Beyond just knowing what is the worst path, slacks tell us **problematic gates** on this path.